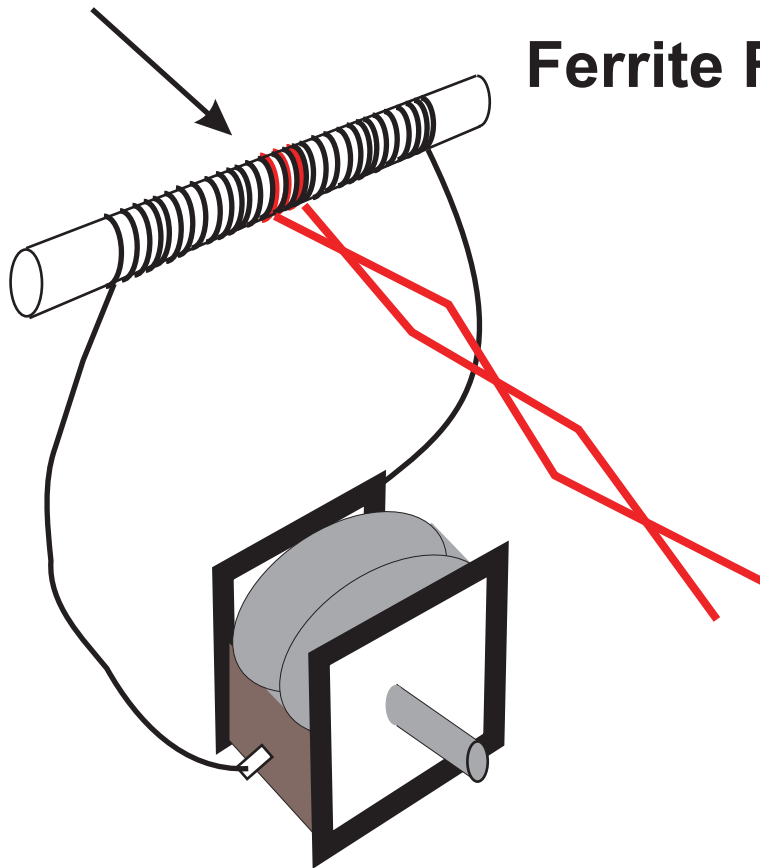


Simple Loop Antenna

4 Turns



Ferrite Rod Antenna

Twisted Pair
to Radio

Variable Capacitor

Use antenna rod and variable cap (approx. 365pF) from 1950's table radio. Wrap four turns of hook-up wire around center of rod. Twist leads (3-6 feet), and attach to antenna and ground terminals of your radio.